

Pipelined CPU Project Report

Omar Rady

December 1st, 2023

CMPEN 331 Final Project with Extra Credit Report

A Pipelined Control Processing Unit with Forwarding

Dr. Mohamed Almekkawy

Device: xczu7eg-ffvf1517-1LV-i

Final Project Extra Credit Report

Table of Contents:


1. Abstract
2. Introduction
3. Waveform 1
4. Waveform 2
5. Design schematics from the RTL of the design
6. I/O planning
7. Floor Planning
8. Pass Implementation proof
9. Pass compilation proof
10. Pass synthesis proof
11. Verilog Source Code
12. Verilog Testbench

Abstract:

This report details the development of an advanced Control Processing Unit (CPU) as part of the Final Project Extra Credit, designed for the XC7Z010-CLG400-1 device. The project expands upon traditional CPU architecture by implementing enhanced features including delayed branching, jumping, and comprehensive support for load/store (LW/SW) operations, I-format, and all R-format instructions, including specific shifting commands like sll. The integration of these features allows for a more versatile and efficient processing unit, capable of handling a broader range of operations with improved performance and flexibility. This extended functionality not only demonstrates a deep understanding of CPU architecture but also aligns with contemporary needs in computer organization and architecture.


Introduction:

In the rapidly evolving field of computer organization, the need for versatile and efficient CPU architectures is paramount. The project presented here introduces a sophisticated CPU design. The CPU's architecture is designed to support delayed branching and jumping, crucial for optimizing instruction pipeline flow and reducing cycle penalties typically associated with branch instructions. The heart of the CPU is its pipelined architecture, which divides the processing into distinct stages, each responsible for a part of the instruction execution process. This pipelining not only increases the throughput of the CPU but also ensures that each instruction is efficiently processed through the system. The addition of forwarding mechanisms and stall control logic addresses the challenges of data hazards and pipeline interruptions, thereby maintaining smooth operation and maximizing performance. In conclusion, the CPU design presented in this report exemplifies a comprehensive approach to modern CPU architecture. Below is a detailed description of what I did to achieve this architecture.

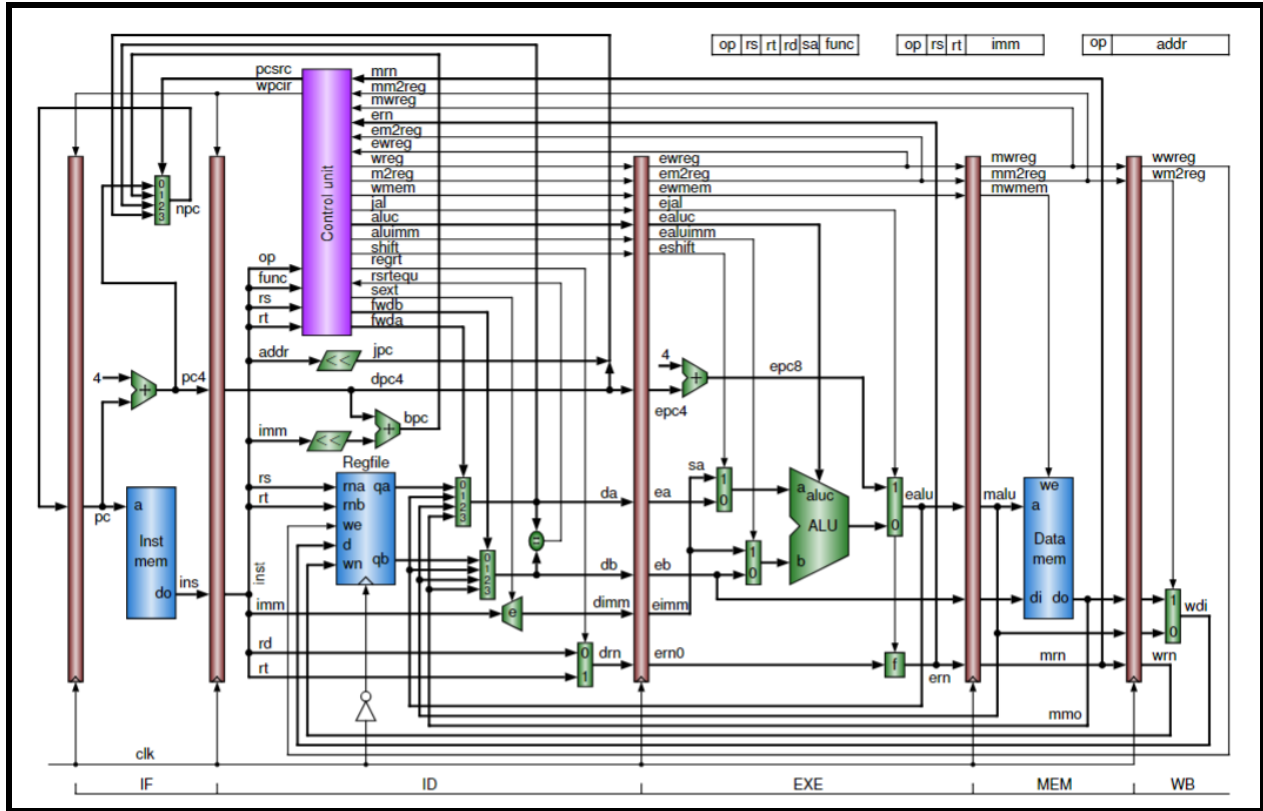


In order to achieve the pipeline architecture with forwarding and delayed branches I had to add some modules on top of the existing architecture of a cpu. For forwarding, I added 2 new muxes that check for forwarding conditions and if they hold true it forwards the value. For delayed branching, shifting and jumping I had to add 8 more modules. The first is a mux that decides what the next program counter value is, which of course changes than the normal +4 when dealing with branches and jumping. Additionally, we needed an immediate extender with concatenation for the jump functionality. When it comes to branching, it also needed it's own adder module and in addition a comparator module in the ID stage to limit the stalls needed. We also added jal muxes to deal with the Jal operation's special needs. Moreover, since our CPU now supports a variety of commands, including shifting, we needed another alu mux to pass in the correct variable to the ALU unit. Finally, we expanded the CPU and ALU operations to allow for the calculation of our delayed branching, jumping, shifting, I-formats, and all R-formats.


Waveform 1:

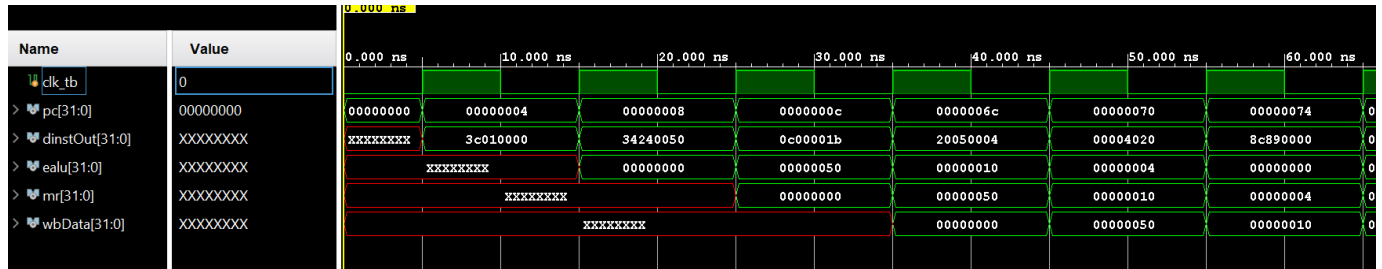

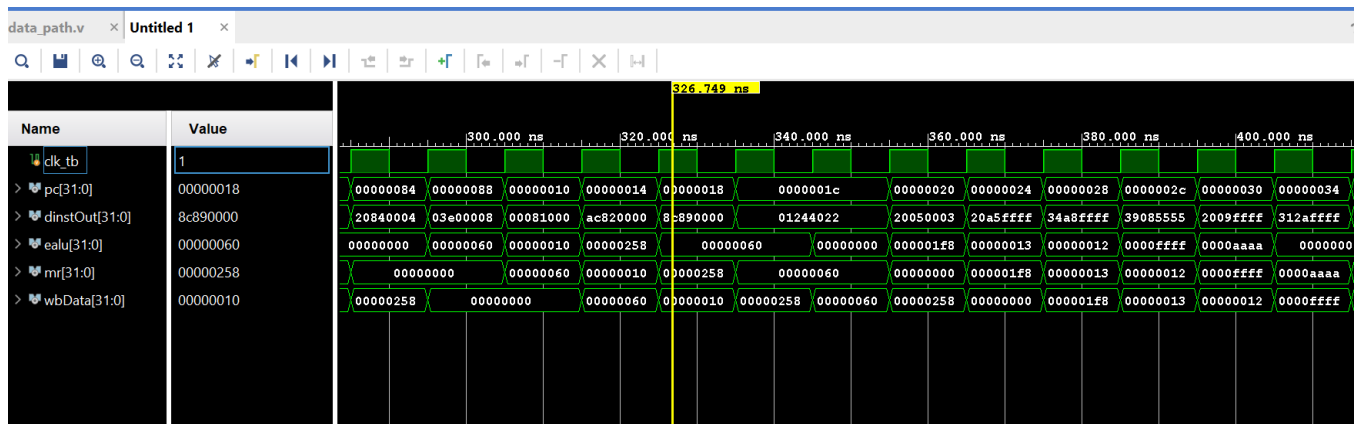Waveform 2: (ram[5'h18] should be 0x00000258, the sum stored by sw instruction, which is instruction 10)




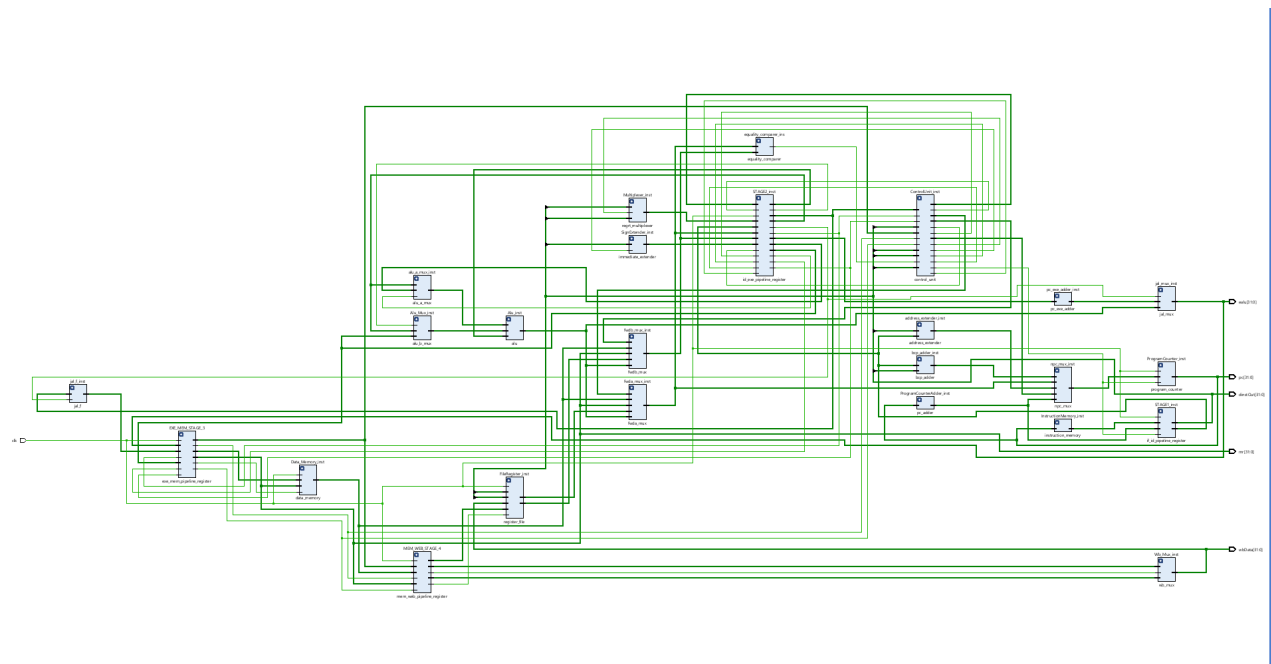Design schematics from the RTL of the design:




I/O planning: (large device with lots of I/O)


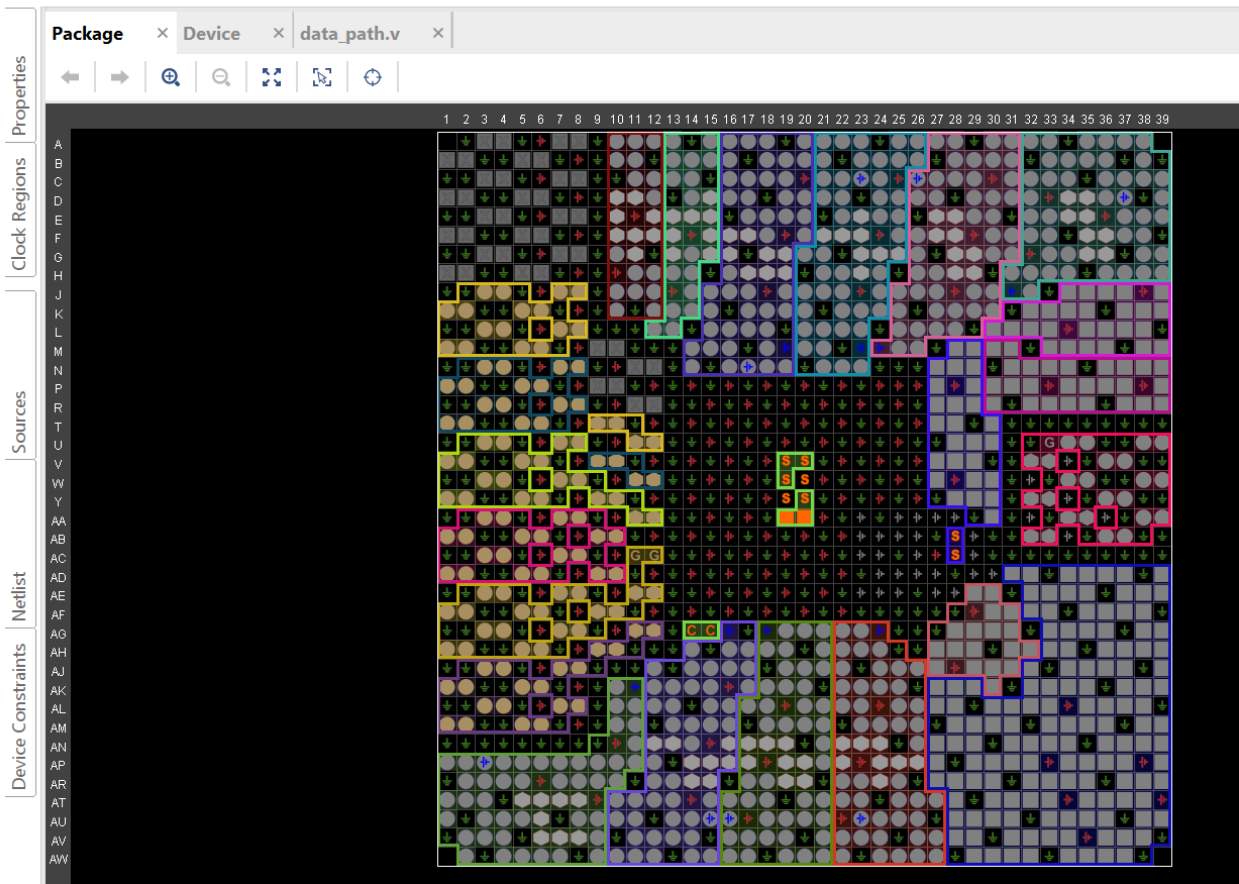
SYNTHESIZED DESIGN - xczu7eg-ffvf1517-1LV-i



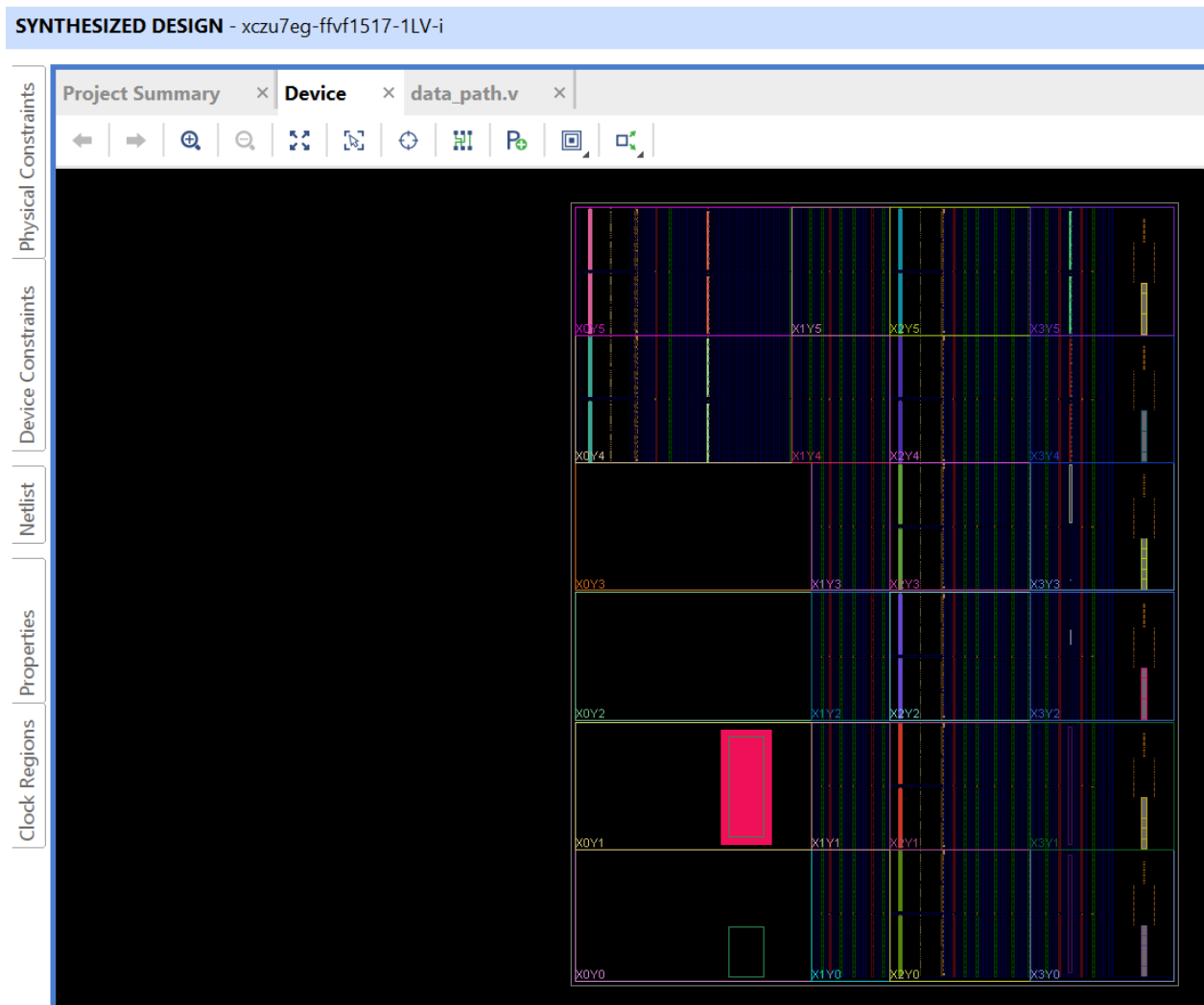Floor Planning: (large device with lots of I/O)




Pass Implementation proof:

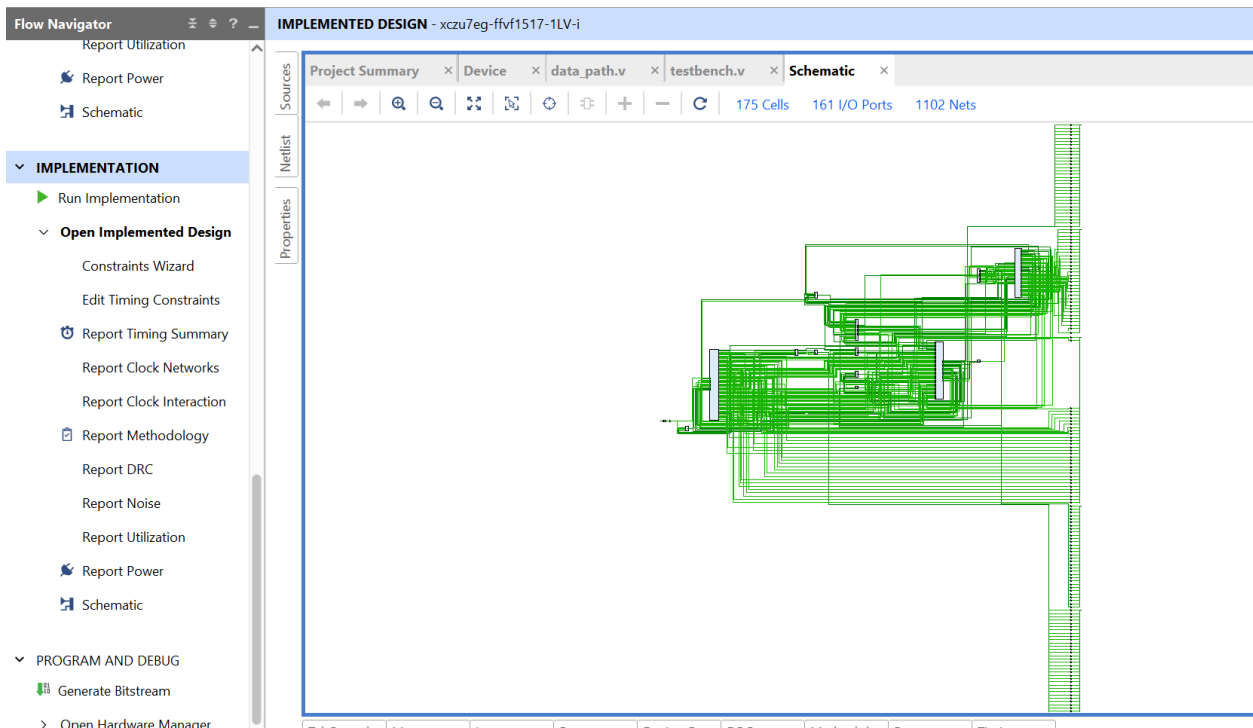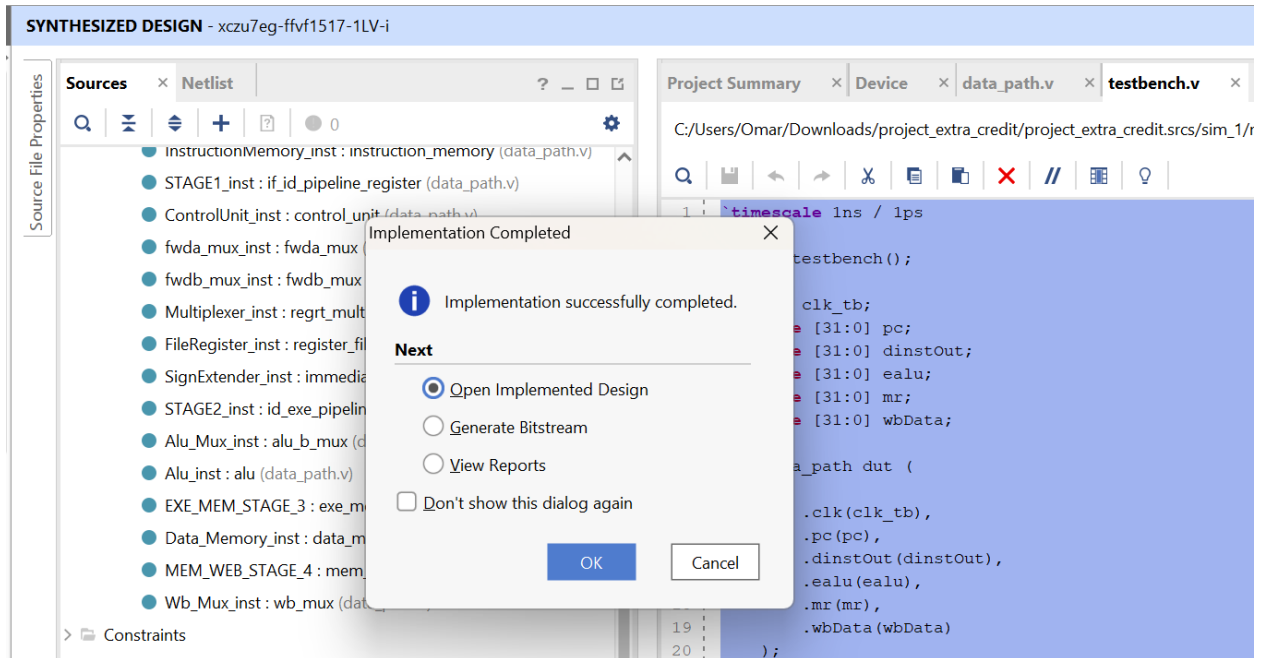

Pass compilation proof:

(proved with waveforms and synthesis and implementation working)

Pass synthesis proof:

 

VERILOG SOURCE CODE:

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////
```

```
// Company: Penn State
```

```
// Engineer: Omar Rady
```

```
//
```

```
// Create Date: 11/10/2023 06:05:55 PM
```

```
// Module Name: cpu data path
```

```
// Project Name: Final Project with Extra Credit
```

```
// Target Devices: XC7Z010-CLG400-1
```

```
// Description: Lab5
```

```
//
```

```
// Dependencies:
```

```

//

// Revision 0.01 - File Created

// Additional Comments:

//

////////////////////////////////////

// MY DATA PATH MODULE WHERE modules are initiated.

module data_path(

    input clk,

    output wire [31:0] pc,

    output wire [31:0] dinstOut,

    output wire [31:0] ealu,

    output wire [31:0] mr,

    output wire [31:0] wbData

);

// wires decoding the instruction

wire [31:0] npc;

wire [31:0] inst_out;

wire [5:0] op;

wire [4:0] rs;

wire [4:0] rt;

wire [4:0] rd;

```

```
wire [4:0] shamt;  
  
wire [5:0] funct;  
  
wire [15:0] imm;  
  
wire [25:0] address;  
  
assign op = dinstOut[31:26];  
  
assign rs = dinstOut [25:21];  
  
assign rt = dinstOut [20:16];  
  
assign rd = dinstOut [15:11];  
  
assign shamt = dinstOut [10:6];  
  
assign funct = dinstOut [5:0];  
  
assign imm = dinstOut [15:0];  
  
assign address = dinstOut [25:0];
```

```
// Internal Wires within IF/ID
```

```
wire wreg;  
  
wire wmem;  
  
wire m2reg;  
  
wire [3:0] aluc;  
  
wire aluimm;  
  
wire regrt;  
  
wire [4:0] destReg;  
  
wire [31:0] qa;  
  
wire [31:0] qb;
```

```
wire [31:0] dqa;  
wire [31:0] dqb;  
wire [31:0] imm32;
```

```
// Internal Wires within ID/EXE
```

```
wire [31:0] b;  
wire [31:0] a;  
wire [1:0] fwda;  
wire [1:0] fwdb;  
wire ewreg;  
wire em2reg;  
wire ewmem;  
wire [3:0] ealuc;  
wire ealuimm;  
wire [4:0] edestReg;  
wire [31:0] eqa;  
wire [31:0] eqb;  
wire [31:0] eimm32;  
wire [31:0] r;
```

```
// wires out of EXE/MEM
```

```
wire mwreg;  
wire mm2reg;
```

```
wire mwmem;  
  
wire [4:0] mdestReg;  
  
wire [31:0] mqb;  
  
wire [31:0] mdo;
```

```
// wires out of MEM/WB
```

```
wire wwreg;  
  
wire wm2reg;  
  
wire [4:0] wdestReg;  
  
wire [31:0] wr;  
  
wire [31:0] wdo;
```

```
// EXTRA CREDIT WIRES TO IMPLMENT SHIFT, JUMP, AND BRANCH
```

```
wire [1:0] pcsrc;  
  
wire wpcir;  
  
wire [31:0] bpc;  
  
wire [31:0] jpc;  
  
wire [31:0] pc4;  
  
wire [31:0] dpc4;  
  
wire [31:0] epc4;  
  
wire [31:0] epc8;  
  
wire rsrtequ;  
  
wire sext;
```

```
wire shift;

wire jal;

wire ejal;

wire eshift;

wire [4:0] edestReg2;
```

```
// EXTRA CREDIT PROJECT MODULES FOR STALLS, DELAYED BRANCHES,
JUMPS, AND SHIFTS
```

```
npc_mux npc_mux_inst(
    .pcsrc(pcsrc),
    .pc4(pc4),
    .bpc(bpc),
    .dqa(dqa),
    .jpc(jpc),
    .npc(npc)
);

address_extender address_extender_inst(
    .address(address),
    .dpc4(dpc4),
    .jpc(jpc)
);

bcp_adder bcp_adder_inst(
```

```
.dpc4(dpc4),  
.imm(imm),  
.bpc(bpc)  
);
```

```
equality_comparer equality_comparer_inst(  
.dqa(dqa),  
.dqb(dqb),  
.rsrtequ(rsrtequ)  
);
```

```
pc_exe_adder pc_exe_adder_inst(  
.epc4(epc4),  
.epc8(epc8)  
);
```

```
alu_a_mux alu_a_mux_inst(  
.eqa(eqa),  
.eimm32(eimm32),  
.eshift(eshift),  
.a(a)  
);
```

```
jal_mux jal_mux_inst(  
    .epc8(epc8),  
    .r(r),  
    .ejal(ejal),  
    .ealu(ealu)  
);
```

```
jal_f jal_f_inst(  
    .edestReg(edestReg),  
    .ejal(ejal),  
    .edestReg2(edestReg2)  
);
```

```
// -----
```

```
// ALL OTHER PREVIOUS OBJECT INSTANSIATIONS
```

```
program_counter ProgramCounter_inst (  
    .clk(clk),  
    .wpcir(wpcir),  
    .npc(npc),  
    .pc(pc)  
);
```



```
pc_adder ProgramCounterAdder_inst (  
    .pc(pc),  
    .pc4(pc4)  
);
```

```
instruction_memory InstructionMemory_inst (  
    .pc(pc),  
    .instOut(inst_out)  
);
```

```
if_id_pipeline_register STAGE1_inst (  
    .clk(clk),  
    .wpcir(wpcir),  
    .instOut(inst_out),  
    .dInstOut(dinstOut),  
    .pc4(pc4),  
    .dpc4(dpc4)  
);
```

```
control_unit ControlUnit_inst (  
    .op(op),  
    .func(func),  
    .wreg(wreg),
```

```
.m2reg(m2reg),  
.wmem(wmem),  
.aluc(aluc),  
.aluimm(aluimm),  
.regrt(regrt),  
// PROJECT ADDITIONS  
.rs(rs),  
.rt(rt),  
.mdestReg(mdestReg),  
.mm2reg(mm2reg),  
.mwreg(mwreg),  
.edestReg(edestReg),  
.em2reg(em2reg),  
.ewreg(ewreg),  
.fwdb(fwdb),  
.fwda(fwda),  
.wpcir(wpcir),  
// Extra Credit  
.pcsrc(pcsrc),  
.rsrtequ(rsrtequ),  
.sext(sext),  
.shift(shift),  
.jal(jal)
```

);

fwda_mux fwda_mux_inst(

.fwda(fwda),

.qa(qa),

.r(r),

.mr(mr),

.mdo(mdo),

.dqa(dqa)

);

fwdb_mux fwdb_mux_inst(

.fwdb(fwdb),

.qb(qb),

.r(r),

.mr(mr),

.mdo(mdo),

.dqb(dqb)

);

regt_mux Multiplexer_inst (

.rt(rt),

.rd(rd),

```
.regrt(regrt),  
.destReg(destReg)  
);
```

```
register_file FileRegister_inst (  
    .rs(rs),  
    .rt(rt),  
    .qa(qa),  
    .qb(qb),  
    .wdestReg(wdestReg),  
    .wbData(wbData),  
    .wwreg(wwreg),  
    .clk(clk)  
);
```

```
immediate_extender SignExtender_inst (  
    .imm(imm),  
    .sext(sext),  
    .imm32(imm32)  
);
```

```
id_exe_pipeline_register STAGE2_inst (  
    .clk(clk),
```

```
.wreg(wreg),  
.ewreg(ewreg),  
.m2reg(m2reg),  
.em2reg(em2reg),  
.wmem(wmem),  
.ewmem(ewmem),  
.aluc(aluc),  
.ealuc(ealuc),  
.aluimm(aluimm),  
.ealuimm(ealuimm),  
.destReg(destReg),  
.edestReg(edestReg),  
.dqa(dqa),  
.eqa(eqa),  
.dqb(dqb),  
.eqb(eqb),  
.imm32(imm32),  
.eimm32(eimm32),  
// EXTRA CREDIT VARIABLES  
.dpc4(dpc4),  
.epc4(epc4),  
.jal(jal),  
.ejal(ejal),
```

```
.shift(shift),  
.eshift(eshift)  
);
```

```
alu_b_mux Alu_Mux_inst (  
    .eqb(eqb),  
    .eimm32(eimm32),  
    .ealuimm(ealuimm),  
    .b(b)  
);
```

```
alu Alu_inst (  
    .a(a),  
    .b(b),  
    .ealuc(ealuc),  
    .r(r)  
);
```

```
exe_mem_pipeline_register EXE_MEM_STAGE_3(  
    .clk(clk),  
    .ewreg(ewreg),  
    .em2reg(em2reg),  
    .ewmem(ewmem),
```

```
.edestReg2(edestReg2),  
.ealu(ealu),  
.eqb(eqb),  
.mwreg(mwreg),  
.mm2reg(mm2reg),  
.mwmem(mwmem),  
.mdestReg(mdestReg),  
.mr(mr),  
.mqb(mqb)  
);
```

```
data_memory Data_Memory_inst(  
    .clk(clk),  
    .mr(mr),  
    .mqb(mqb),  
    .mwmem(mwmem),  
    .mdo(mdo)  
);
```

```
mem_web_pipeline_register MEM_WEB_STAGE_4(  
    .clk(clk),  
    .mwreg(mwreg),  
    .mm2reg(mm2reg),
```

```
.mdestReg(mdestReg),  
  
.mr(mr),  
  
.mdo(mdo),  
  
.wwreg(wwreg),  
  
.wm2reg(wm2reg),  
  
.wdestReg(wdestReg),  
  
.wr(wr),  
  
.wdo(wdo)  
);
```

```
wb_mux Wb_Mux_inst(  
  
.wr(wr),  
  
.wdo(wdo),  
  
.wm2reg(wm2reg),  
  
.wbData(wbData)  
);
```

```
endmodule
```

```
// ----- STAGE 1: INSTRUCTION FETCH -----
```

```
module program_counter(  

```



```

input clk, input wire wpcir,

input wire [31:0] npc, output reg [31:0] pc

);

initial begin

    pc = 32'd0;

end

always @(posedge clk) begin

    if (wpcir) begin pc <= npc; end

end

endmodule

```

```

module instruction_memory(input wire [31:0] pc, output reg [31:0] instOut); // CHANGE TO
LW INSTRUCTIONS

    wire [31:0] rom [0:63];

    // rom[word_addr] = instruction // (pc) label instruction

    assign rom[6'h00] = 32'h3c010000; // (00) main: lui $1, 0

    assign rom[6'h01] = 32'h34240050; // (04) ori $4, $1, 80

    assign rom[6'h02] = 32'h0c00001b; // (08) call: jal sum

    assign rom[6'h03] = 32'h20050004; // (0c) dslot1: addi $5, $0, 4

    assign rom[6'h04] = 32'hac820000; // (10) return: sw $2, 0($4)

    assign rom[6'h05] = 32'h8c890000; // (14) lw $9, 0($4)

    assign rom[6'h06] = 32'h01244022; // (18) sub $8, $9, $4

```

```
assign rom[6'h07] = 32'h20050003; // (1c) addi $5, $0, 3
assign rom[6'h08] = 32'h20a5ffff; // (20) loop2: addi $5, $5, -1
assign rom[6'h09] = 32'h34a8ffff; // (24) ori $8, $5, 0xffff
assign rom[6'h0a] = 32'h39085555; // (28) xori $8, $8, 0x5555
assign rom[6'h0b] = 32'h2009ffff; // (2c) addi $9, $0, -1
assign rom[6'h0c] = 32'h312affff; // (30) andi $10,$9,0xffff
assign rom[6'h0d] = 32'h01493025; // (34) or $6, $10, $9
assign rom[6'h0e] = 32'h01494026; // (38) xor $8, $10, $9
assign rom[6'h0f] = 32'h01463824; // (3c) and $7, $10, $6
assign rom[6'h10] = 32'h10a00003; // (40) beq $5, $0, shift
assign rom[6'h11] = 32'h00000000; // (44) dslot2: nop
assign rom[6'h12] = 32'h08000008; // (48) j loop2
assign rom[6'h13] = 32'h00000000; // (4c) dslot3: nop
assign rom[6'h14] = 32'h2005ffff; // (50) shift: addi $5, $0, -1
assign rom[6'h15] = 32'h000543c0; // (54) sll $8, $5, 15
assign rom[6'h16] = 32'h00084400; // (58) sll $8, $8, 16
assign rom[6'h17] = 32'h00084403; // (5c) sra $8, $8, 16
assign rom[6'h18] = 32'h000843c2; // (60) srl $8, $8, 15
assign rom[6'h19] = 32'h08000019; // (64) finish: j finish
assign rom[6'h1a] = 32'h00000000; // (68) dslot4: nop
assign rom[6'h1b] = 32'h00004020; // (6c) sum: add $8, $0, $0
assign rom[6'h1c] = 32'h8c890000; // (70) loop: lw $9, 0($4)
assign rom[6'h1d] = 32'h01094020; // (74) stall: add $8, $8, $9
```

```

    assign rom[6'h1e] = 32'h20a5ffff; // (78) addi $5, $5, -1
    assign rom[6'h1f] = 32'h14a0fffc; // (7c) bne $5, $0, loop
    assign rom[6'h20] = 32'h20840004; // (80) dslot5: addi $4, $4, 4
    assign rom[6'h21] = 32'h03e00008; // (84) jr $31
    assign rom[6'h22] = 32'h00081000; // (88) dslot6: sll $2, $8, 0

    always @(*) begin
        instOut = rom[pc / 4];
    end

endmodule

```

```

module pc_adder(input wire [31:0] pc, output reg [31:0] pc4);

    always @(*) begin
        pc4 = pc + 32'd4;
    end

endmodule

```

```

module if_id_pipeline_register(
    input clk,
    input wire wpcir,
    input wire [31:0] instOut,
    output reg [31:0] dInstOut,

```

```

    input wire [31:0] pc4,
    output reg [31:0] dpc4
);

always @(posedge clk) begin
    if (wpcir) begin
        dInstOut <= instOut;
        dpc4 <= pc4;
    end
end

endmodule

```

```

module npc_mux( // EXTRA CREDIT PROJECT MODULES FOR DELAYED BRANCHES
    input wire [1:0] pcsrc,
    input wire [31:0] pc4,
    input wire [31:0] bpc,
    input wire [31:0] dqa,
    input wire [31:0] jpc,
    output reg [31:0] npc
);

always @(*) begin
    if(pcsrc==0) begin npc = pc4; end
    if(pcsrc==1) begin npc = bpc; end

```

```

        if(pcsrc==2) begin npc = dqa; end

        if(pcsrc==3) begin npc = jpc; end

    end

endmodule


// ----- STAGE 2: INSTRUCTION DECODE -----


module control_unit(
    input wire [5:0] op,
    input wire [5:0] func,
    output reg wreg,
    output reg m2reg,
    output reg wmem,
    output reg [3:0]aluc,
    output reg aluimm,
    output reg regrt,

    // PROJECT ADDITIONS
    input wire [4:0] rs,
    input wire [4:0] rt,
    input wire [4:0] mdestReg,
    input wire mm2reg,
    input wire mwreg,

```

```

input wire [4:0] edestReg,

input wire em2reg,

input wire ewreg,

output reg [1:0] fwdb,

output reg [1:0] fwda,

output reg wpcir,

// EXTRA CREDIT VARIABLES

output reg [1:0] pcsrc,

input wire rsrtequ,

output reg jal,

output reg shift,

output reg sext

);

initial begin wpcir = 1'b1; pcsrc = 2'b00; end

// STALL LOGIC

reg stall = 1'b0;

reg i_rs = 1'b0;

reg i_rt = 1'b0;

always @(*) begin

    wpcir = 1'b1;

    shift = 0;

    if(op == 6'b000000) begin i_rs = 1'b1; i_rt = 1'b1; end

    if(op == 6'b100011) begin i_rs = 1'b1; i_rt = 1'b0; end

```

```
stall = ewreg & em2reg & (edestReg!=0) & (i_rs & (edestReg == rs) | i_rt & (edestReg ==  
rt));
```

```
if(stall) begin // NEED TO PREVENT WRITE
```

```
    wpcir = 1'b0;
```

```
    wreg = 0;
```

```
    m2reg = 0;
```

```
    wmem = 0;
```

```
    aluc = 4'b0000;
```

```
end
```

```
else begin
```

```
case(op)
```

```
    6'b000000: begin // R-TYPE Instructions
```

```
        wreg = 1;
```

```
        m2reg = 0;
```

```
        wmem = 0;
```

```
        aluimm = 0;
```

```
        regrt = 0;
```

```
        jal = 0;
```

```
        pcsrc = 2'b00;
```

```
        case(func)
```

```
            6'b100000: aluc = 4'b0010; // add
```

```
            6'b100010: aluc = 4'b0110; // sub
```

```
            6'b100100: aluc = 4'b0000; // and
```

```

        6'b100101: aluc = 4'b0001; // or
        6'b100110: aluc = 4'b0011; // xor

        6'b000000: begin aluc = 4'b1010; shift = 1; end // sll
        6'b000010: begin aluc = 4'b1100; shift = 1; end // srl
        6'b000011: begin aluc = 4'b1011; shift = 1; end // sra
        6'b001000: pcsrc = 2'b10; // jr

        // Additional R-TYPE instructions if needed

    endcase

end

// ----- I-FORMATS -----

6'b001000: // addi command

begin

    wreg = 1;

    regrt = 1;

    m2reg = 0;

    wmem = 0;

    aluc = 4'b0010; // Add

    aluimm = 1;

    sext = 1; // Sign extend the immediate

    jal = 0;

    pcsrc = 2'b00;

end

6'b001100: // andi command

```



```

begin

    wreg = 1;

    regrt = 1;

    wmem = 0;

    m2reg = 0;

    aluc = 4'b0000; // And

    aluimm = 1;

    sext = 0;

    jal = 0;

    pcsrc = 2'b00;

end

6'b001101: // ori command

begin

    wreg = 1;

    regrt = 1;

    wmem = 0;

    m2reg = 0;

    aluc = 4'b0001; // OR

    aluimm = 1;

    sext = 0;

    jal = 0;

    pcsrc = 2'b00;

end

```

```
6'b001110: // xori command
```

```
begin
```

```
    wreg = 1;
```

```
    regrt = 1;
```

```
    wmem = 0;
```

```
    m2reg = 0;
```

```
    aluc = 4'b0011; // XOR
```

```
    aluimm = 1;
```

```
    sext = 0;
```

```
    jal = 0;
```

```
    pcsrc = 2'b00;
```

```
end
```

```
6'b100011: // lw command
```

```
begin
```

```
    wreg = 1;
```

```
    regrt = 1;
```

```
    m2reg = 1;
```

```
    wmem = 0;
```

```
    aluc = 4'b0010;
```

```
    aluimm = 1;
```

```
    sext = 1;
```

```
    jal = 0;
```

```
    pcsrc = 2'b00;
```

```

end

6'b101011: // sw command

begin

    wreg = 0;

    regrt = 1;

    m2reg = 0;

    wmem = 1;

    aluc = 4'b0010;

    aluimm = 1;

    sext = 1;

    jal = 0;

    pcsrc = 2'b00;

end

6'b000100: // beq command

begin

    wreg = 0;

    m2reg = 0;

    wmem = 0;

    aluc = 4'b0110; // Subtract for comparison

    aluimm = 0;

    jal = 0;

    pcsrc = rsrtequ ? 2'b01 : 2'b00; // Branch if rs and rt are equal

end

```

```
6'b000101: // bne command
```

```
begin
```

```
    wreg = 0;
```

```
    m2reg = 0;
```

```
    wmem = 0;
```

```
    aluc = 4'b0110; // Subtract for comparison
```

```
    aluimm = 0;
```

```
    jal = 0;
```

```
    pcsrc = rsrtequ ? 2'b00 : 2'b01; // Branch if rs and rt are not equal
```

```
end
```

```
6'b001111: // lui command
```

```
begin
```

```
    pcsrc = 2'b00;
```

```
    wreg = 1;
```

```
    m2reg = 0;
```

```
    wmem = 0;
```

```
    aluc = 4'b0100; // Operation for LUI
```

```
    aluimm = 1;
```

```
    sext = 0;
```

```
    jal = 0;
```

```
end
```

```
// ----- j format -----
```

```
6'b000010: // j command
```

```

begin
    wreg = 0;
    m2reg = 0;
    wmem = 0;
    aluimm = 0;
    aluc = 4'b0000;
    pcsrc = 2'b11;
    jal = 0;
end

6'b000011: // jal command
begin
    m2reg = 0;
    wmem = 0;
    aluimm = 0;
    aluc = 4'b0000;
    pcsrc = 2'b11;
    wreg = 1;
    jal = 1;
end

endcase end

end

// FINAL PROJECT FORWARDING UNIT

always @(*) begin

```

```

// Default no forwarding

fwda = 2'b00;

fwdb = 2'b00;


// Forwarding logic for ALU operand A (rs)
if (ewreg && (edestReg == rs) && !em2reg) begin

    // Forward from ALU result in EX stage

    fwda = 2'b01;

end else if (mwreg && (mdestReg == rs) && !mm2reg) begin

    // Forward from ALU result in MEM stage

    fwda = 2'b10;

end else if (mwreg && (mdestReg == rs) && mm2reg) begin

    // Forward from data memory (load-use hazard)

    fwda = 2'b11;

end


// Forwarding logic for ALU operand B (rt)
if (ewreg && (edestReg == rt) && !em2reg) begin

    // Forward from ALU result in EX stage

    fwdb = 2'b01;

end else if (mwreg && (mdestReg == rt) && !mm2reg) begin

    // Forward from ALU result in MEM stage

    fwdb = 2'b10;

end

```

```

        end else if (mwreg && (mdestReg == rt) && mm2reg) begin

            // Forward from data memory (load-use hazard)

            fwd_b = 2'b11;

        end

    end

endmodule

```

```

module regrt_mux(
    input wire [4:0] rt,
    input wire [4:0] rd,
    input wire regrt,
    output reg [4:0] destReg
);

    always @(*) begin
        if(regrt==0)
            begin
                destReg = rd;
            end
        if(regrt==1)
            begin
                destReg = rt;
            end
    end

end

```

```
endmodule
```

```
module register_file(  
    input wire [4:0] rs,  
    input wire [4:0] rt,  
    output reg [31:0] qa,  
    output reg [31:0] qb,  
    // UPDATED REG GETS ADDITIONAL PARAMETERS:  
    input [4:0] wdestReg,  
    input [31:0] wbData,  
    input wwreg,  
    input clk  
);  
    reg [31:0] register [0:31];  
    integer i;  
    initial begin  
        for (i = 0; i < 32; i = i + 1) begin  
            register[i] = 32'h00000000;  
        end  
    end  
    always @(*)  
        begin  
            qa = register[rs];
```



```

        qb = register[rt];
    end
always @(negedge clk)
begin
    if(wwreg == 1) begin
        register[wdestReg] = wbData;
    end
end
endmodule

```

```

module immediate_extender(input wire [15:0] imm, input wire sext, output reg [31:0] imm32);
    always @(*)
    begin
        if (sext)
            imm32 = {{16{imm[15]}}}, imm};
        else
            imm32 = {16'b0, imm};
        end
    endmodule

```

```

module id_exe_pipeline_register(
input clk,
input wreg,      output reg ewreg,

```

```

input  m2reg,      output reg em2reg,
input  wmem,       output reg ewmem,
input  [3:0] aluc,  output reg [3:0] ealuc,
input  aluimm,     output reg ealuimm,
input  [4:0] destReg, output reg [4:0] edestReg,
input  [31:0] dqa,  output reg [31:0] eqa,
input  [31:0] dqb,  output reg [31:0] eqb,
input  [31:0] imm32, output reg [31:0] eimm32,

```

```
// EXTRA CREDIT VARIABLES
```

```

input [31:0] dpc4, output reg [31:0] epc4,
input jal, output reg ejal,
input shift, output reg eshift
);

```

```
always @(posedge clk)
```

```
begin
```

```
    ewreg <= wreg;
```

```
    em2reg <= m2reg;
```

```
    ewmem <= wmem;
```

```
    ealuc <= aluc;
```

```
    ealuimm <= aluimm;
```

```
    edestReg <= destReg;
```

```
    eqa <= dqa;
```

```
    eqb <= dqb;
```

```

        eimm32 <= imm32;

        epc4 <= dpc4;

        ejal <= jal;

        eshift <= shift;

    end

endmodule


// FINAL PROJECT 2 NEW Muxes

module fwda_mux(
    input wire [1:0] fwda,
    input wire [31:0] qa,
    input wire [31:0] r,
    input wire [31:0] mr,
    input wire [31:0] mdo,
    output reg [31:0] dqa
);

    always @(*) begin

        if(fwda==0) begin dqa = qa; end

        if(fwda==1) begin dqa = r; end

        if(fwda==2) begin dqa = mr; end

        if(fwda==3) begin dqa = mdo; end

    end

endmodule

```

```

module fwdb_mux(
input wire [1:0] fwdb,
input wire [31:0] qb,
input wire [31:0] r,
input wire [31:0] mr,
input wire [31:0] mdo,
output reg [31:0] dqb
);

always @(*) begin
    if(fwdb==0) begin dqb = qb; end
    if(fwdb==1) begin dqb = r; end
    if(fwdb==2) begin dqb = mr; end
    if(fwdb==3) begin dqb = mdo; end
end
endmodule

```

// EXTRA CREDIT MODULES

```

module address_extender(
    input wire [25:0] address,
    input wire [31:0] dpc4,
    output reg [31:0] jpc
);

```

```

always @(*)
    begin
        jpc = {dpc4[31:28], address[25:0], 2'b00};
    end
endmodule

```

```

module bcp_adder(
    input wire [31:0] dpc4,
    input wire [15:0] imm,
    output reg [31:0] bpc
);
    wire [31:0] imm_extended = {{16{imm[15]}}}, imm};
    always @(*)
        begin
            bpc = dpc4 + (imm_extended << 2);
        end
endmodule

```

```

module equality_comparer(
    input wire [31:0] dqa,
    input wire [31:0] dqb,
    output reg rsrtequ
);

```

```

always @(*)
    begin
        if(dqa == dqb) begin rsrtequ = 1; end
        else begin rsrtequ = 0; end
    end
endmodule

// ----- STAGE 3: EXE Stage -----

module alu_b_mux(
    input [31:0] eqb,
    input [31:0] eimm32,
    input ealuimm,
    output reg [31:0] b
);
always @(*)
    begin
        if(ealuimm == 0)
            begin
                b = eqb;
            end
        if(ealuimm == 1)
            begin

```

```

        b = eimm32;
    end
end
endmodule

module alu(
    input [31:0] a,
    input [31:0] b,
    input [3:0] ealuc,
    output reg [31:0] r
);
    always @(*)
    begin
        case (ealuc)
            4'b0010: r = a + b;           // Add
            4'b0110: r = a - b;           // Subtract
            4'b0000: r = a & b;           // AND
            4'b0001: r = a | b;           // OR
            4'b0011: r = a ^ b;           // XOR
            4'b1010: r = b << a[4:0];     // Shift left logical (sll)
            4'b1100: r = b >> a[4:0];     // Shift right logical (srl)
            4'b1011: r = $signed(b) >>> a[4:0]; // Shift right arithmetic (sra)
            4'b0100: r = b << 16;         // Load Upper Immediate (lui)

```

```

        default: r = 32'b0;           // Default output value
    endcase

end

endmodule

```

```

module exe_mem_pipeline_register(

    input clk,

    // Inputs

    input ewreg,

    input em2reg,

    input ewmem,

    input [4:0] edestReg2,

    input [31:0] ealu,

    input [31:0] eqb,

    // Outputs

    output reg mwreg,

    output reg mm2reg,

    output reg mwmem,

    output reg [4:0] mdestReg,

    output reg [31:0] mr, // also called malu

    output reg [31:0] mqb

);

always @(posedge clk)

```



```

begin

    mwreg <= ewreg;

    mm2reg <= em2reg;

    mwmem <= ewmem;

    mdestReg <= edestReg2;

    mr <= ealu;

    mqb <= eqb;

end

endmodule


// EXTRA CREDIT MODULES

module pc_exe_adder(input wire [31:0] epc4, output reg [31:0] epc8);

    always @(*)

        begin

            epc8 = epc4 + 32'd4;

        end

endmodule


module alu_a_mux(

    input wire [31:0] eqa,

    input wire [31:0] eimm32,

    input wire eshift,

    output reg [31:0] a

```

```

);

always @(*)
    begin
        if(eshift) begin a = {27'b0, eimm32[10:6]}; end
        else begin a = eqa; end
    end
endmodule

```

```

module jal_mux(
    input wire [31:0] epc8,
    input wire [31:0] r,
    input ejal,
    output reg [31:0] ealu
);

always @(*)
    begin
        if(ejal) begin ealu = epc8; end
        else begin ealu = r; end
    end
endmodule

```

```

module jal_f(
    input wire [4:0] edestReg,

```

```

    input wire ejal,

    output reg [4:0] edestReg2

);

always @(*)

    begin

        if(ejal) begin edestReg2 = 5'd31; end

        else begin edestReg2 = edestReg; end

    end

endmodule

```

```

// ----- STAGE 4: MEMORY -----

```

```

module data_memory(

    input clk,

    input [31:0] mr,

    input [31:0] mqb,

    input mwmem,

    output reg [31:0] mdo

);

// MY MEMORY

reg [31:0] ram [63:0];

```

```

integer i;

initial begin

    for (i = 0; i < 32; i = i + 1)

        ram[i] = 0;

    // ram[word_addr] = data // (byte_addr) item in data array

    ram[5'h14] = 32'h000000a3; // (50) data[0] 0 + a3 = a3
    ram[5'h15] = 32'h00000027; // (54) data[1] a3 + 27 = ca
    ram[5'h16] = 32'h00000079; // (58) data[2] ca + 79 = 143
    ram[5'h17] = 32'h00000115; // (5c) data[3] 143 + 115 = 258

    // ram[5'h18] should be 0x00000258, the sum stored by sw instruction

end

always @(*) begin

    mdo = ram[mr / 4];

end

always @(posedge clk) begin

    if(mwmem) begin

        ram[mr / 4] <= mqb;

    end

end

endmodule

module mem_web_pipeline_register(

    input clk,    // Clock signal

```

```

// Inputs

input mwreg,    // Control signal for writing to the register

input mm2reg,   // Control signal for choosing source for register write-back

input [4:0] mdestReg, // Destination register address

input [31:0] mr, // Memory address for read

input [31:0] mdo, // Output data from memory

// Outputs

output reg wwreg,    // Control signal for writing to the register

output reg wm2reg,   // Control signal for choosing source for register write-back

output reg [4:0] wdestReg, // Destination register address for write-back

output reg [31:0] wr, // Register address for read-back

output reg [31:0] wdo // Data to write back to the register

);

always @(posedge clk) begin

    wwreg    <= mwreg;

    wm2reg   <= mm2reg;

    wdestReg <= mdestReg;

    wr       <= mr;

    wdo      <= mdo;

end

endmodule

// ----- LAB 5: WB Modules -----

```

```

module wb_mux(
    input [31:0] wr,
    input [31:0] wdo,
    input wm2reg,
    output reg [31:0] wbData
);

always @(*) begin
    if(wm2reg == 1) begin
        wbData = wdo;
    end
    if(wm2reg == 0) begin
        wbData = wr;
    end
end

endmodule

```

VERILOG TESTBENCH CODE:

```

`timescale 1ns / 1ps

```

```

module testbench();

```

```

    reg clk_tb;

```

```

    wire [31:0] pc;

```

```
wire [31:0] dinstOut;

wire [31:0] ealu;

wire [31:0] mr;

wire [31:0] wbData;


data_path dut (

    .clk(clk_tb),

    .pc(pc),

    .dinstOut(dinstOut),

    .ealu(ealu),

    .mr(mr),

    .wbData(wbData)

);


initial begin

    clk_tb = 0;

end

always begin

    #5 clk_tb = !clk_tb;

end

endmodule
```

